

Assignment 1

Question 1: Design a BCD-to-decimal decoder.

Question 2: A combinational circuit is defined by the following three Boolean functions. Design the circuit with a decoder and external gates.

$$F1 = x'y'z' + xz$$

$$F2 = xy'z' + x'y$$

$$F3 = x'y'z + xy$$

Question 3: A combinational circuit is specified by the following three Boolean functions. Implement the circuit with a 3×8 decoder constructed with NAND gates (similar to Fig. 5-10) and three external NAND gates. Use a block diagram for the decoder.

$$F1(A, B, C) = (2, 4, 7)$$

$$F2(A, B, C) = \Sigma(0, 3)$$

$$F3(A, B, C) = \Sigma(0, 2, 3, 4, 7)$$

Question 4: Implement the Boolean function $F(A,B,C,D) = \Sigma(0, 2, 3, 4, 8, 10, 14, 15)$ with an 8×1 multiplexer, but with inputs A, B, and C connected to selection inputs S_2, S_1 , and so, respectively.

Question 5: Assume we want to design full adder circuit with x, y, z as inputs and S and C as outputs. Design it using multiplexers with x and z as select lines.